

Lab 5: Algebraic Operations


Examples and Deliverables

MAE 405, 2025 Spring


TA: Xinlei Zhang

To be prepared with OPAMP

- OPAMP (Operational Amplifier)

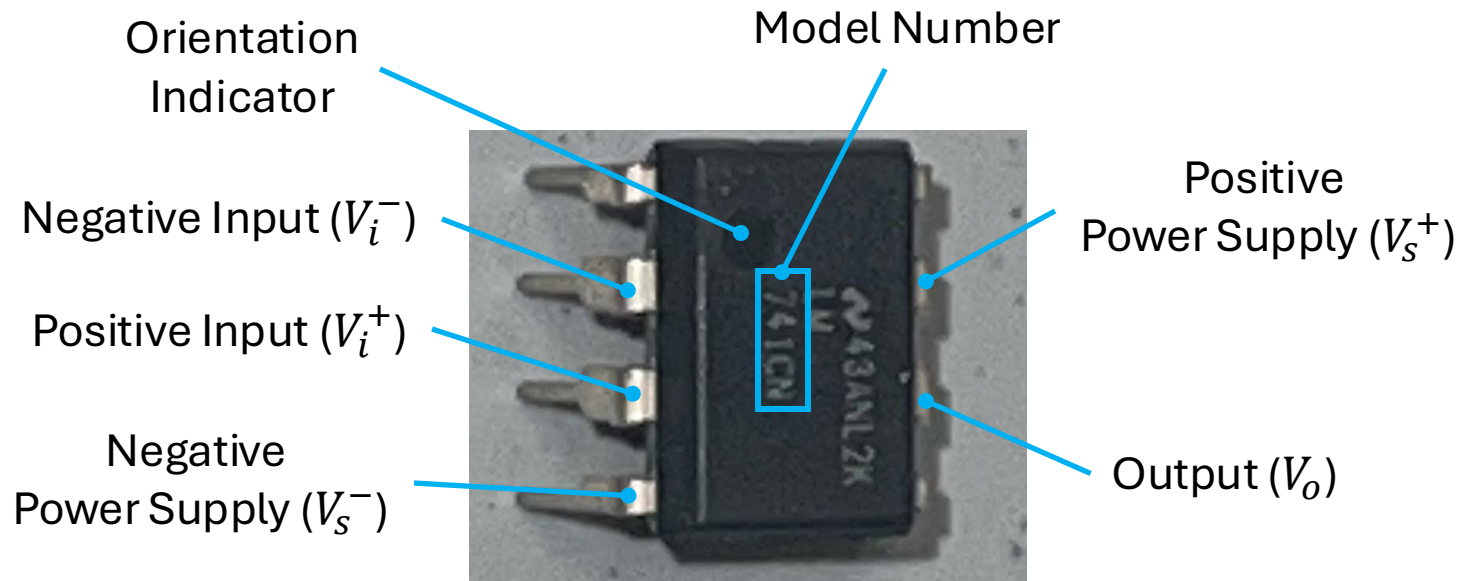

OPAMP 741CN

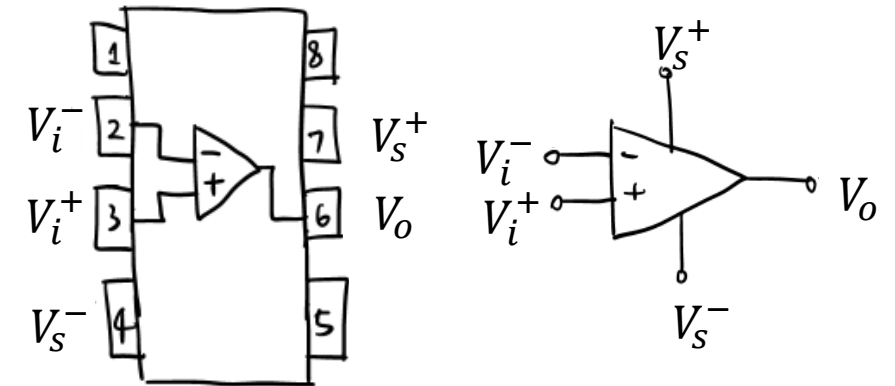



OPAMP Diagram

Comments:

- Put the Circle (orientation indicator) at the upper-left corner to align the OPAMP with the diagram
- Identify the Model Number – 741CN

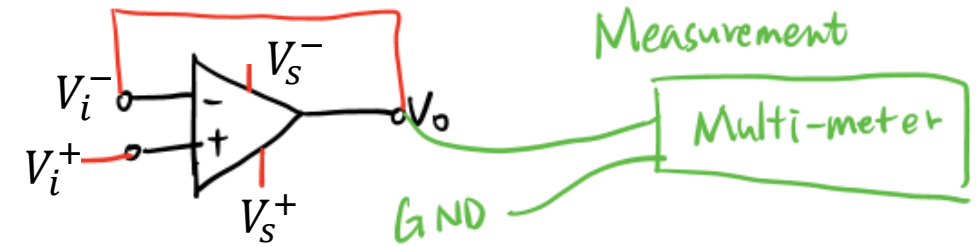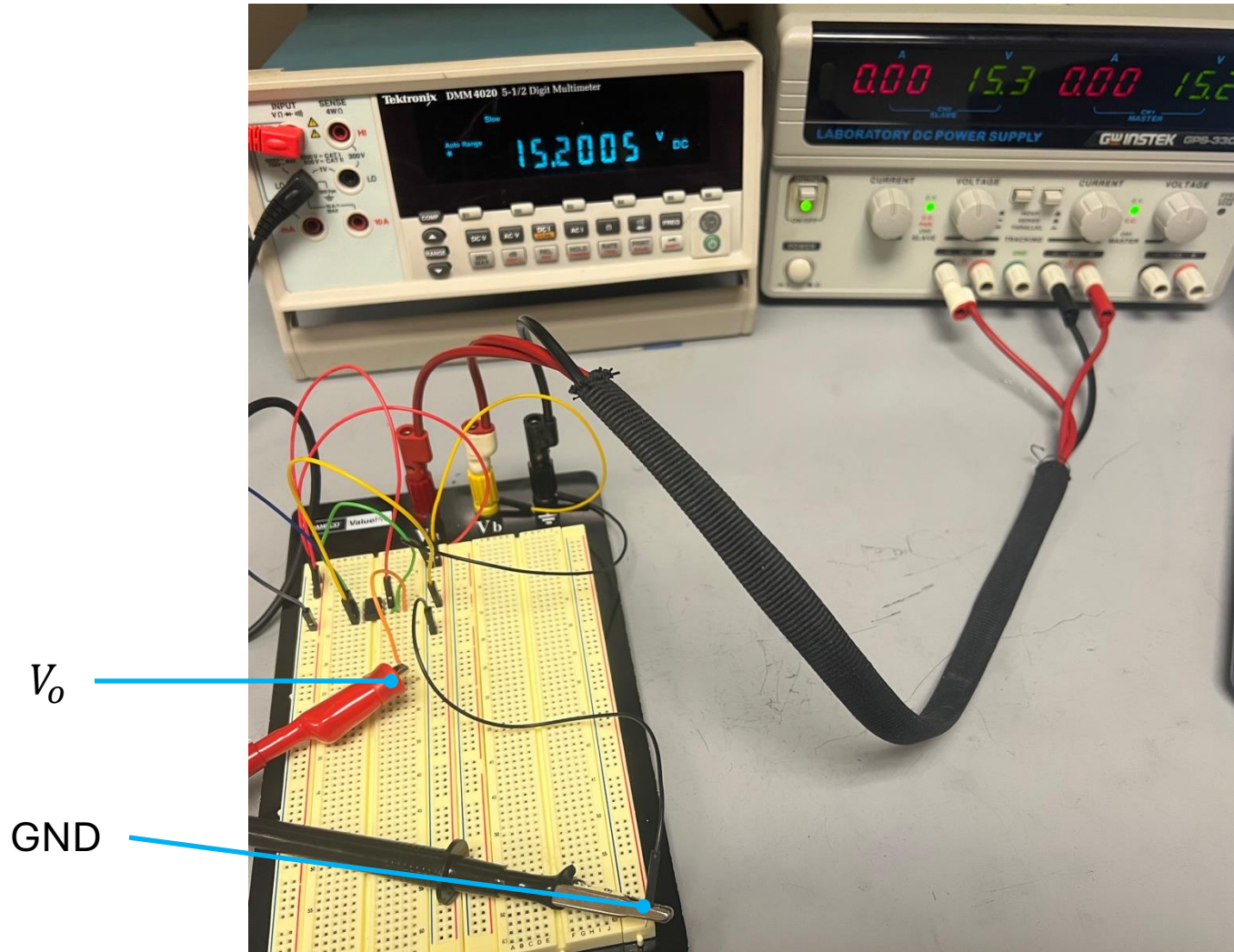Example 1 (Deliverable 1 – Task A in Experiment 4)


- Buffer Circuit – buffering +15V from the power source



Connection Diagram


Expect Result: multimeter red input ($V_o = +15\text{ V}$) – multimeter black input (0 V) = +15 V

Example 1 – Cont'd

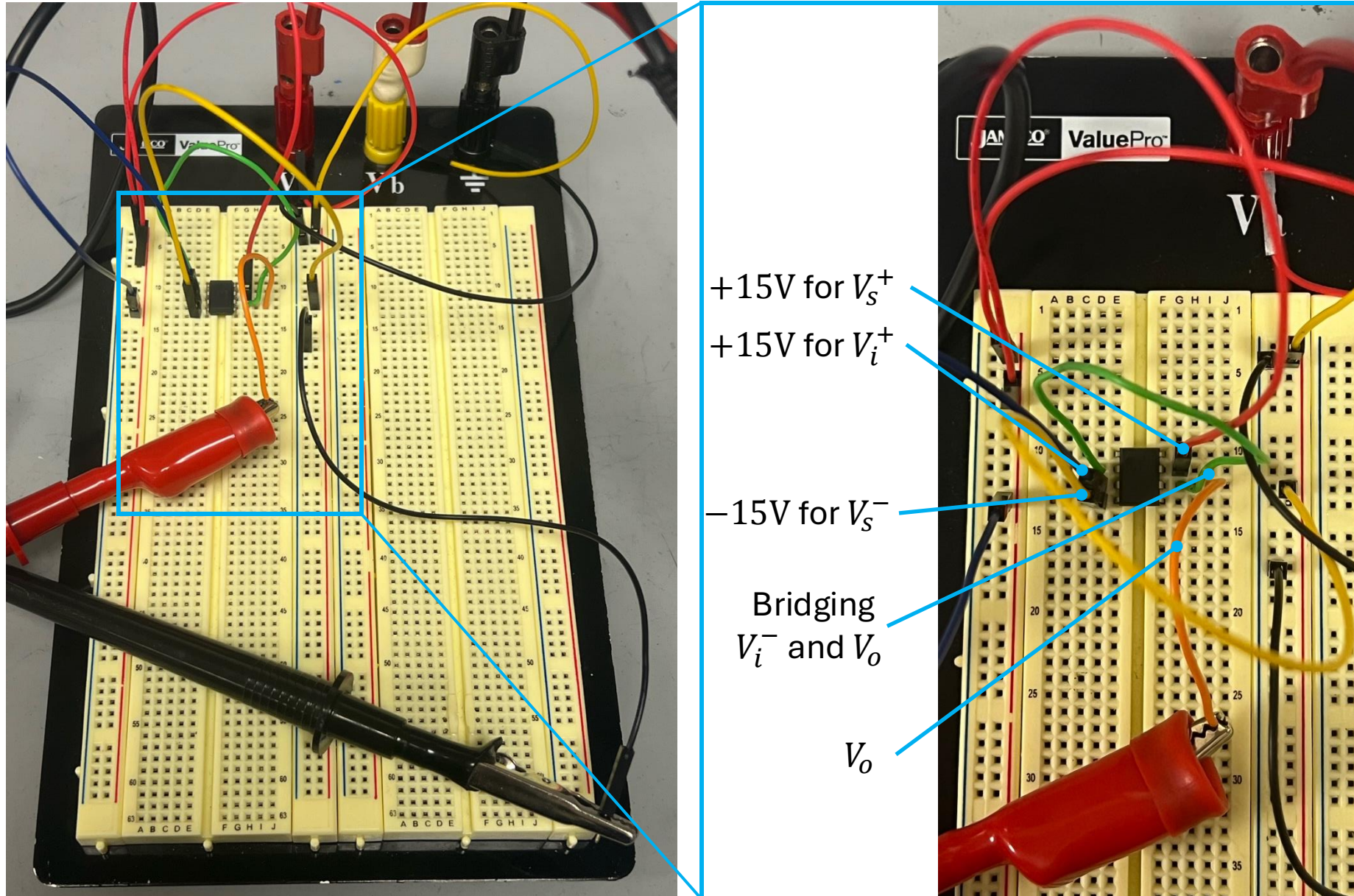

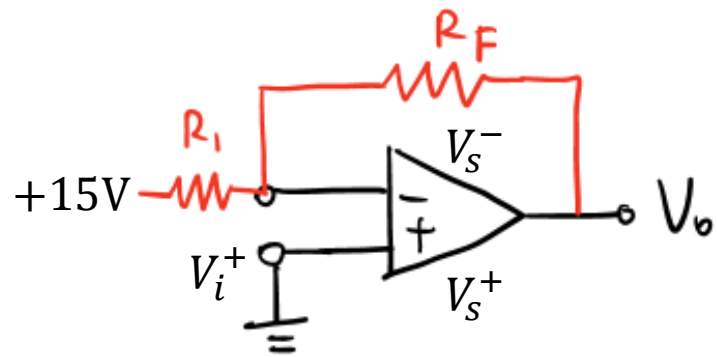Example 2 (Deliverable 2 – Task B in Experiment 4)

- Gain circuit
- To be prepared: get one OPAMP and two resistors (R_F and R_1)
 - To get $V_o = -5V$ from the output of last circuit ($V_o = +15V$ from the buffering circuit)



$$V_o = -\frac{R_F}{R_1} \times 15V$$

- How to select R_F and R_1 ?
As long as $\frac{R_F}{R_1} \approx \frac{1}{3}$, e.g., $R_F = 100 \text{ K}\Omega$, $R_1 = 300 \text{ K}\Omega$
- How to tell the resistance of a resistor?
Multimeter Ohm mode; Color rings




100 KΩ (brown, black, yellow)




300 KΩ (orange, black, yellow)

Example 2 – Cont'd

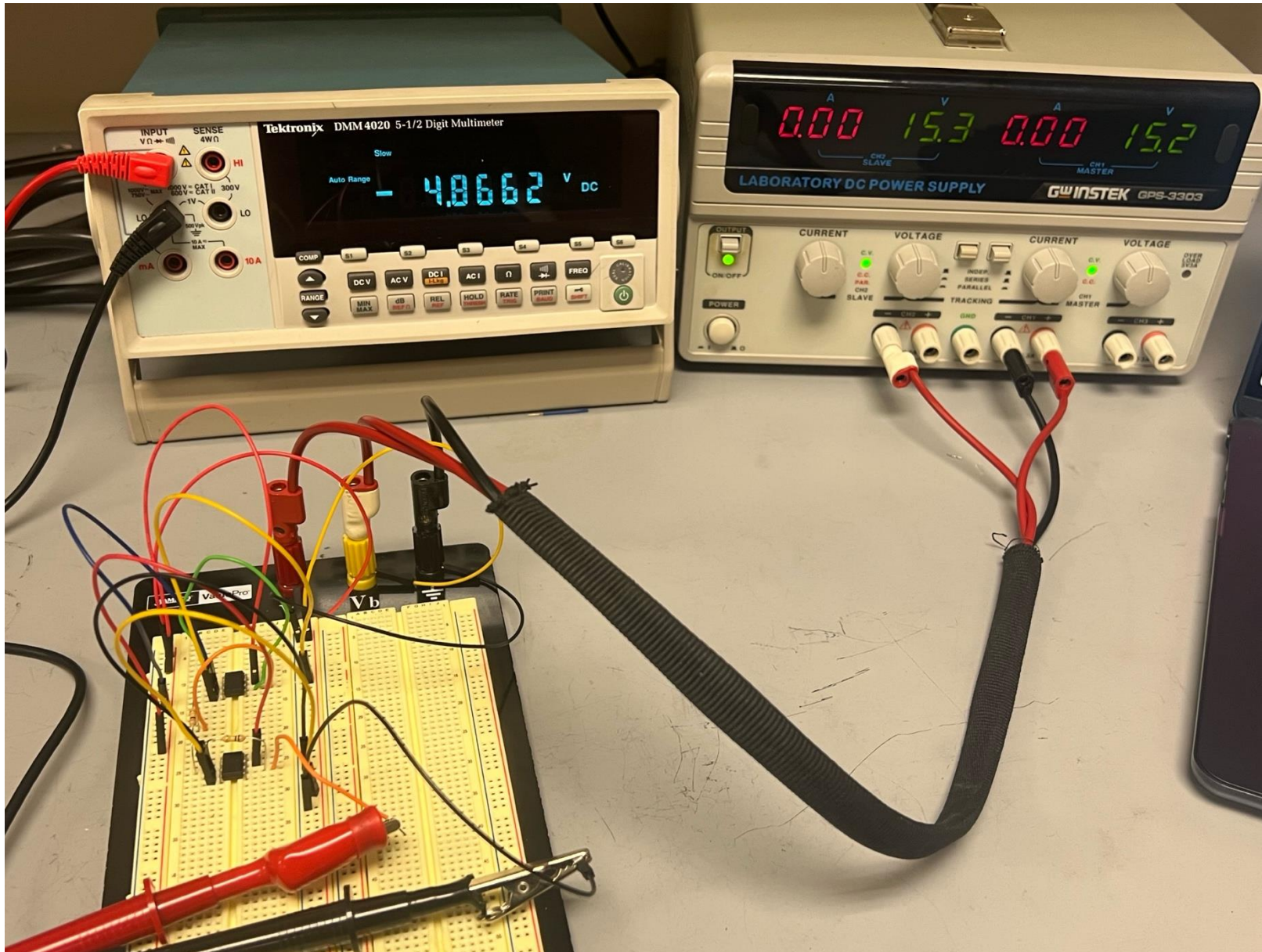

Expect Result: multimeter red input ($V_o = -5V$) – multimeter black input (0V) = $-5V$

Example 2 – Cont'd

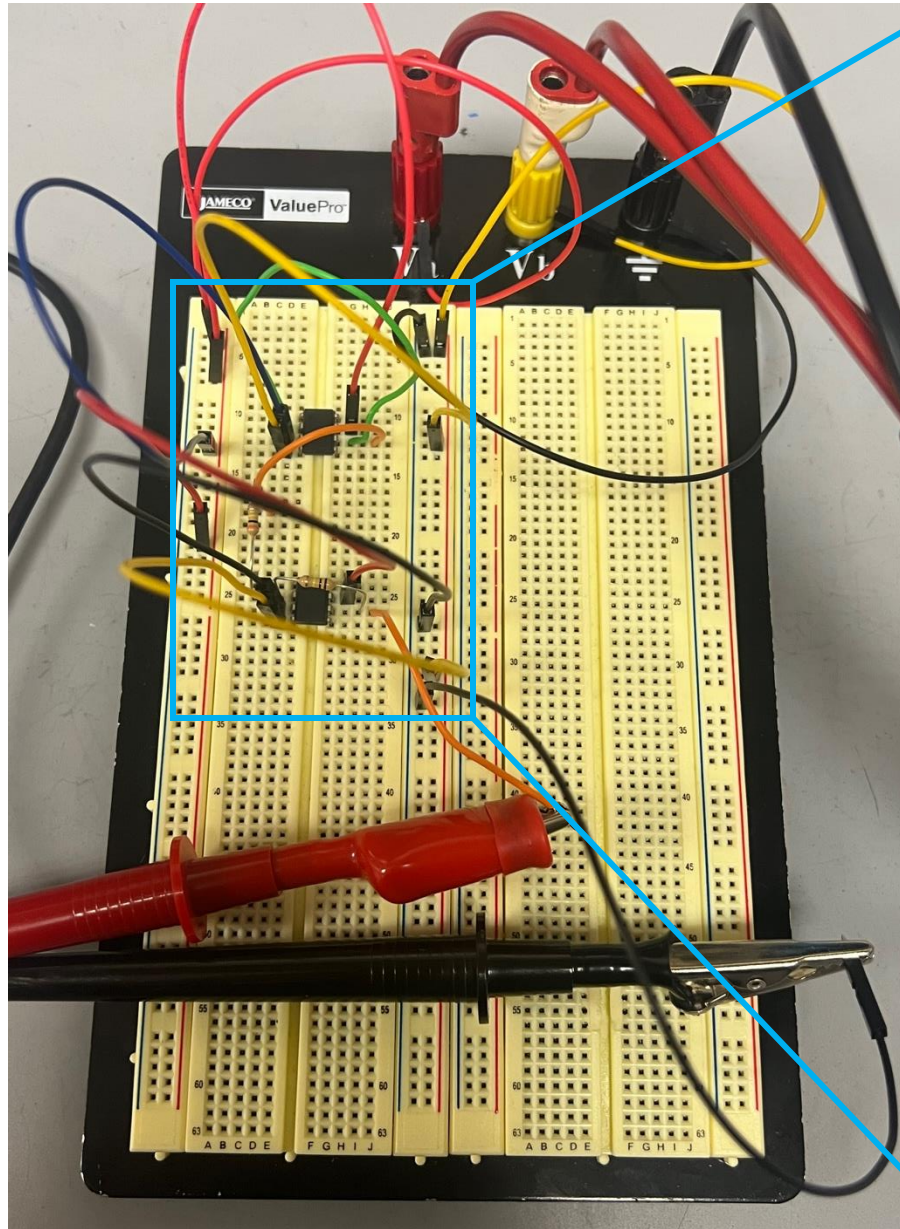

$$V_o = +15 \text{ V}$$


$$R_1 = 300 \text{ k}\Omega$$

$$R_F = 100 \text{ k}\Omega$$

$$0 \text{ V for } V_i^+$$

$$-15 \text{ V for } V_s^-$$

$$V_o$$

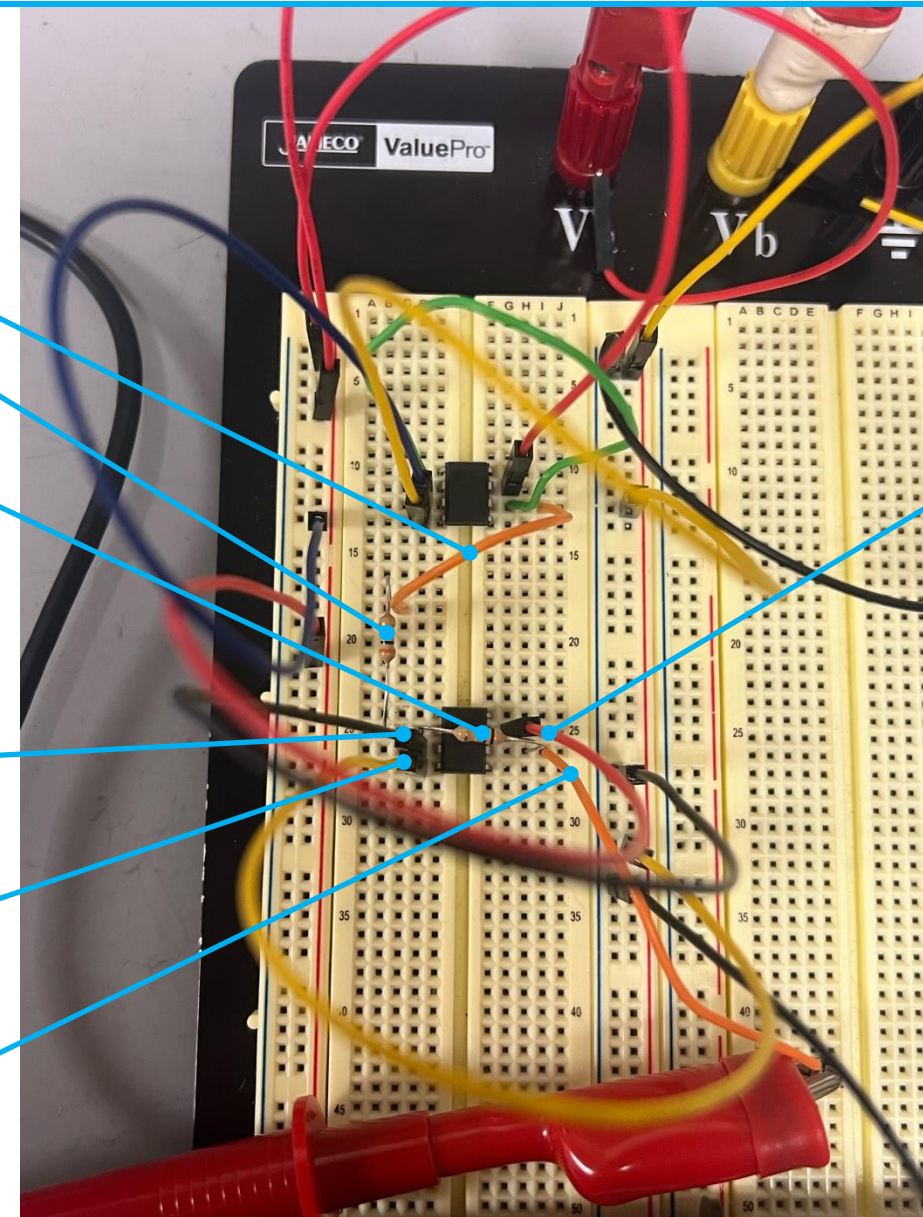


$$+15 \text{ V for } V_s^+$$

Deliverable 3 – Task C in Experiment 4

- Summation of the outputs from circuit A and B

Addition

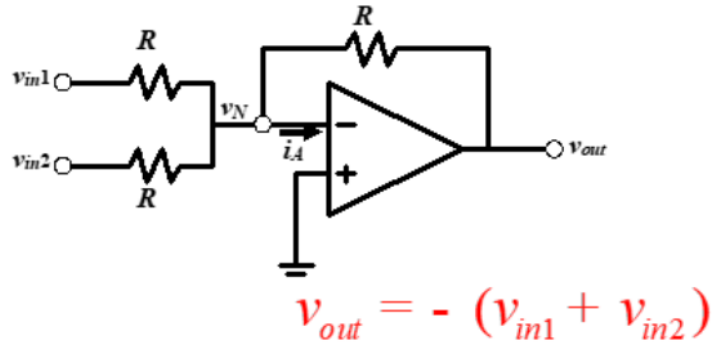

Deliverables Summary:

- Tasks A, B, C, D, E in Experiment 4
- Task F is not required

Deliverable 4 – Task D in Experiment 4

- Invert the output from circuit B
- With the gain circuit, but with gain $\frac{R_F}{R_1} = 1$

Deliverable 5 – Task E in Experiment 4

- Subtraction between the outputs from circuit A and D (A-D)

Subtraction

